

**UNIVERSITY OF NORTH CAROLINA AT CHARLOTTE**  
**Department of Electrical and Computer Engineering**


**EXPERIMENT 1 – BJT DIFFERENTIAL PAIR AMPLIFIER  
WITH BJT CURRENT MIRROR**

**OBJECTIVES**

In this experiment the students will be familiarize with the biasing and operation of a BJT differential pair amplifier.

**INTRODUCTION**

The typical BJT differential pair amplifier consists of a pair of transistors coupled at the emitters to a current source, having equal resistances in each collector and equal but opposite, signal sources in each base. The amplifier has several variations on this basic configuration. The basic configuration (Figure 1-1) will be studied in this experiment.

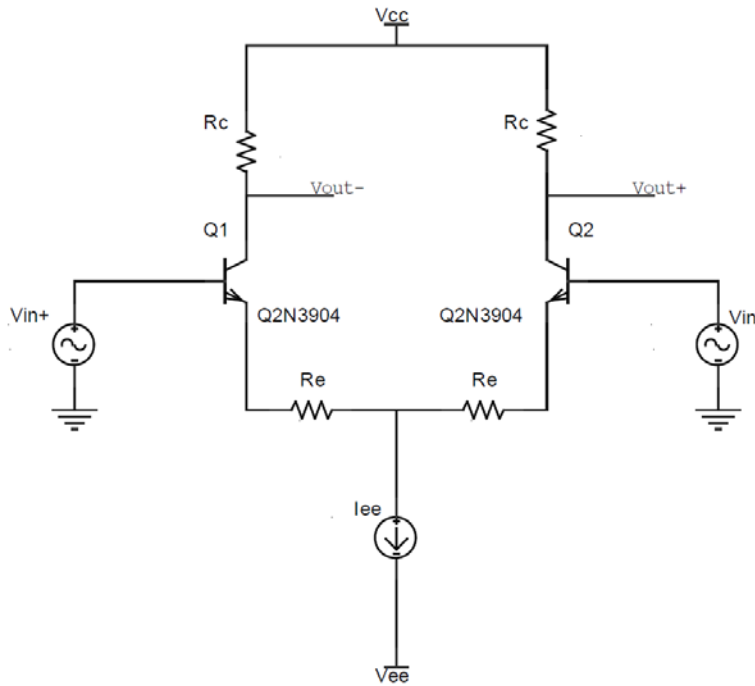

**Figure 1-1 Basic BJT differential pair amplifier**

The important characteristics for the differential pair amplifier to be studied in this experiment are: differential voltage gain ( $A_{vd}$ ), common mode gain ( $A_{vcm}$ ), common-mode rejection ration CMRR, and single-ended voltage gain ( $A_{Vse}$ ).

Assuming that  $r_{o1,2} \gg R_C$  and  $r_{e1} = r_{e2}$ , the following information can be found for the differential pair BJT amplifier:

$$V_{in} = V_{in}(+) + V_{in}(-)$$

$$V_{out}(-) = -i_{c1}R_c = -\alpha i_{e1}R_c \quad \text{and} \quad V_{out}(+) = -i_{c2}R_c = -\alpha i_{e2}R_c$$

$$i_{e1} = \frac{V_{in}}{2r_{e1} + 2R_e} \quad \text{and} \quad i_{e2} = \frac{V_{in}}{2r_{e2} + 2R_e}$$

$$A_{vd} = \frac{V_{out}(+) - V_{out}(-)}{V_{in}(+) - V_{in}(-)} = \frac{\alpha \left( \left( \frac{V_{in}}{2} \right) \frac{R_c}{r_e + R_e} - \left( - \left( \frac{V_{in}}{2} \right) \frac{R_c}{r_e + R_e} \right) \right)}{V_{in}} = \frac{\alpha R_c}{r_e + R_e}$$

**Note:**  $V_{in}(+)$  and  $V_{in}(-)$  are equal and opposite – and add together to make  $V_{in}$ .

The single-ended gain (output taken at either  $V_{out}(+)$  or  $V_{out}(-)$ , is then:

$$A_{vse} = \frac{V_{out}(+)}{V_{in}(-)} = \frac{V_{out}(-)}{V_{in}(+)} = \frac{1}{2} A_{vd} = \frac{\alpha R_c}{2r_e + 2R_e}$$

These results are derived by looking at the output current  $i_c$  flowing through the resistors  $R_c$ , its relation to  $i_e$ , and finding the resultant voltage at the output terminals (in small signal terms).

The common mode gain is found by applying the input signal to both the (+) and (-) inputs to the differential pair as shown in Figure 1-2. The differential output voltage with a common mode input is zero since:

$$V_{out}(+) = V_{out}(-) = -V_{cm} \left( \frac{\alpha R_c}{r_e + R_e + 2r_{ee}} \right)$$

and

$$A_{vcm} = V_{out}(+) - V_{out}(-) = 0$$

However, the single-ended common-mode voltage gain is not zero and is given by:

$$A_{vcmse} = \frac{V_{out}(+)}{V_{cm}} = \frac{V_{out}(-)}{V_{cm}} = \frac{-\alpha R_c}{r_e + R_e + 2r_{ee}}$$

**\*Note:** The term  $2r_{ee}$  is derived from the resistance of the current source  $i_{ee}$  which is ideally infinity, but in practical circuits is not infinitely high.

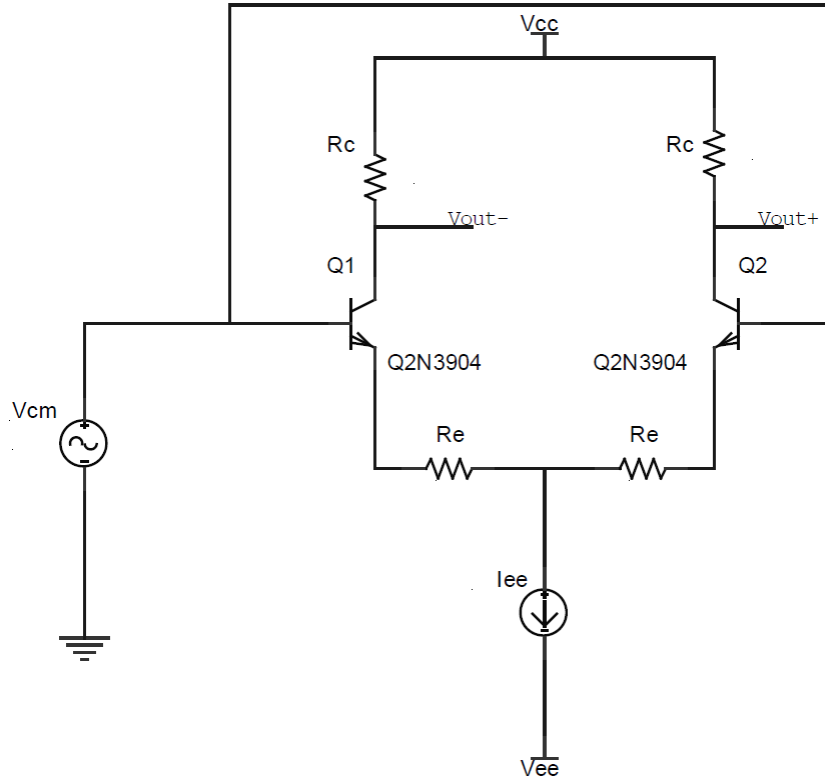


Figure 1-2 Common mode circuit for differential pair


The common-mode rejection ratio is defined by the division of the single-ended differential circuit gain by the single-ended common-mode gain as follows:

$$CMRR = \frac{A_{Vdse}}{A_{Vcmse}} = \frac{\frac{\alpha R_c}{2r_e + 2R_e}}{\frac{\alpha R_c}{r_e + R_e + 2r_{ee}}} = \frac{r_e + R_e + 2r_{ee}}{2r_e + 2R_e} \approx \frac{r_{ee}}{r_e + R_e} \text{ since } r_{ee} \gg r_e + R_e$$

From the above equations it can be seen that the differential amplifier enhances the difference between the inputs and suppresses the common mode component. This desirable characteristic is used to attenuate unwanted presences in the input signal such as noise from a coaxial cable or from an audio cable.

**PRELAB**


1. For the circuit of Figure 1-3, find the values of  $R_{ref}$  and  $R_C$ 's such that  $I_{CQ,A,B}$  is approximately equal to 2 mA and  $V_{CE1,2} = 6V$ . Given:  $V_{CC} = -V_{EE} = 15V$ ,  $R_A = R_B = 2.2k\Omega$ , and  $R_e = 250\Omega$ . Assume:  $V_{BEon} = 0.7V$ ,  $V_t = 25mV$ ,  $V_A = 100V$ ,  $\beta = 100$ ,  $I_{CQ1,2} = 0.5I_{CQ,A,B}$ , and the transistors are matched and operating in the active region.
2. Using the equations in the Introduction and information from the previous part of the prelab, find the small-signal differential voltage gain  $A_{Vd}$ , the differential circuit single-ended gain  $A_{Vse}$ , the single-ended circuit common-mode voltage gain  $A_{Vcmse}$ , and the CMRR (Common-Mode Rejection Ratio) for the circuit in Figure 1-3. The value of  $r_{ee}$  is needed to calculate the CMRR. To determine  $r_{ee}$  assume that the emitter resistor on the reference side of the current mirror is zero. Although this will cause some error it will greatly simplify the calculation.

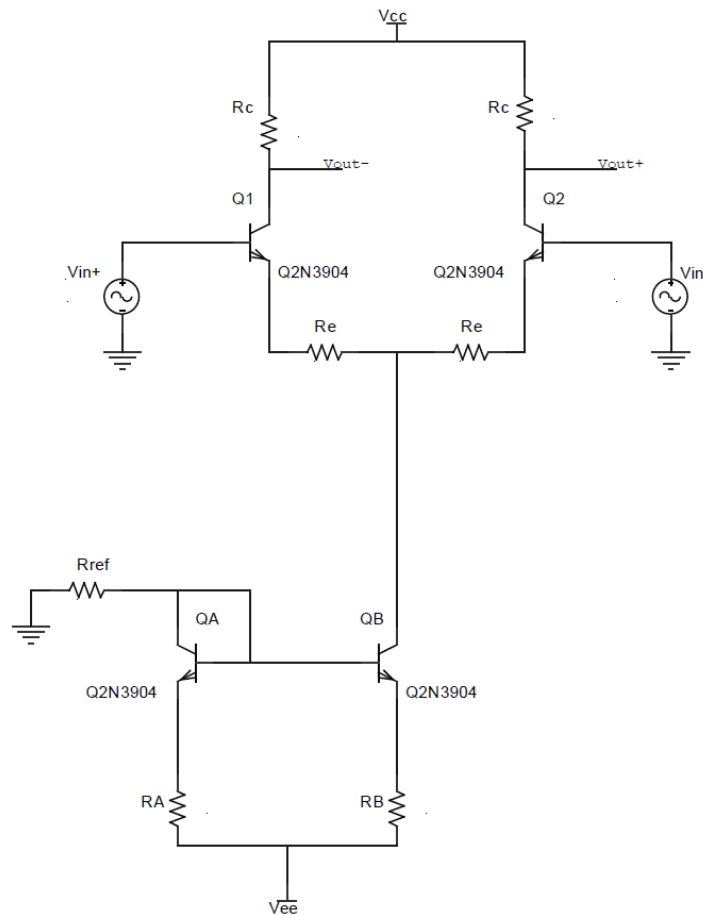

**Figure 1-3 Differential pair amplifier with current mirror biasing**

**PROCEDURE**

1. Prepare the power supplies for  $V_{CC}$  and  $V_{EE}$  to ensure the proper voltages, +15V and -15V, respectively.
2. Connect the circuit of Figure 1-4 with the resistor values calculated in the Prelab. Make sure to include the supply bypass capacitors to reduce noise.

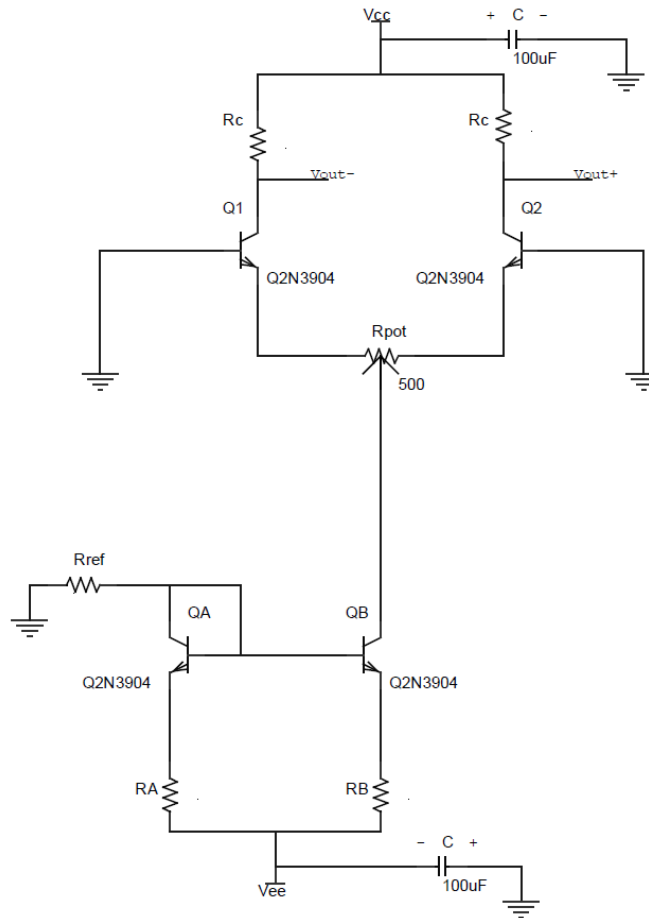

**Figure 1-4 Differential pair amplifier biasing configuration**

3. Measure  $I_{CQA}$ ,  $I_{CQB}$ ,  $V_{CE1}$ , and  $V_{CE2}$ . If  $V_{CE1,2}$  is not equal to approximately 6V, but  $I_{CQA,B} = 2\text{mA}$  and  $V_{BE1,2} \sim 0.7\text{V}$ , adjust  $R_{pot}$  until  $V_{CE1,2}$  is almost 6V. Due to the differences in resistors  $R_C$  and the differences in  $\beta$ , the potentiometer is necessary to balance the differential pair.
4. Record the bias voltages and currents and momentarily take out the potentiometer  $R_{pot}$  and measure the resistance on each side. Measure and record the value of  $I_{CQ1,2}$  and  $V_{C1,2}$ .
5. Apply a small signal input of  $100\text{mV}_{p-p}$  with a frequency of 1kHz at the base of  $Q_1$  (i.e.  $V_{in(+)} = 100\text{mV}_{p-p}$ ). Use a voltage divider as shown in Figure 1-5 below. Leave  $V_{in(-)}$  grounded.
6. Measure and record the single-ended output voltages  $V_{out(+)}$  and  $V_{out(-)}$ . Note which is in phase and which is out of phase with  $V_{in(+)}$ .

- Vary the function generator frequency and record enough data to plot the voltage gain ( $A_{V_{se}} = V_{out}/V_{in}$ ) versus frequency. Do this only for the  $V_{out(-)}$  output point, it is not necessary to take measurements for both as they will have the same frequency response.

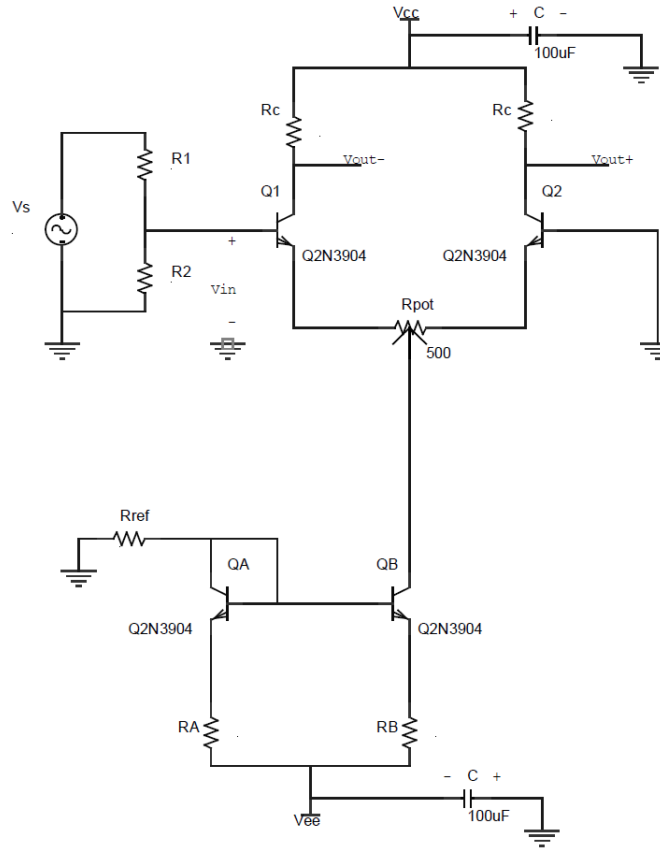


Figure 1-5 Differential amplifier with single-ended input ( $R_1 \& R_2 \gg r_{inQ1}$ )

- Now connect the small signal input to  $V_{in(-)}$  and ground  $V_{in(+)}$ . Again use a voltage divider network to attain a  $100mV_{p-p}$  input with a frequency of  $1kHz$  at  $V_{in(-)}$ .
- Now measure and record the single-ended output voltages  $V_{out(+)}$  and  $V_{out(-)}$ . Note which is in phase and which is out of phase with  $V_{in(-)}$ .
- Vary the function generator frequency and record enough data to plot the voltage gain ( $A_{V_{se}} = V_{out}/V_{in}$ ) versus frequency. For the same reason as before, only do this for the  $V_{out(+)}$  output point.
- Using the same circuit used in step 10, connect channel 1 of the oscilloscope to  $V_{out(+)}$  and channel 2 of the oscilloscope to  $V_{out(-)}$ . Make sure that the volts/division adjustments are the same for both channels. This will allow for the calculation of the differential voltage gain:

$$A_{vd} = \frac{V_{out(+)} - V_{out(-)}}{V_{in}}$$

- Vary the function generator frequency in order to obtain enough data to plot the differential voltage gain  $A_{vd}$  versus frequency.

13. Now connect a sinusoidal input ( $4.0V_{p-p}$  @ 1kHz) to both  $V_{in(+)}$  and  $V_{in(-)}$ , this connection will allow for common-mode measurements.
14. Measure and record the single-ended common-mode output voltage at either  $V_{out(+)}$  or  $V_{out(-)}$ . Vary the function generator frequency and record enough data to plot the single-ended common-mode voltage gain  $A_{V_{cmse}}$  versus frequency.

## POST-LAB

Post-Lab questions must be answered in each experiment's laboratory report.

1. Plot voltage gain vs. frequency for the data collected in Steps 7, 10 and 14 of the Procedure using Excel, Matlab or a similar software. Compare the plots and note any differences. Do the different configurations have a similar frequency response? Did the voltage gains for each circuit at 1kHz correspond to the calculated values from the Prelab?
2. Using the data obtained for the single-ended common-mode gain and the differential circuit single-ended gain (either measurement), calculate the Common Mode Rejection Ratio (CMRR) for the differential pair amplifier. Compare this with the calculated value in the Prelab.
3. Did the calculated bias currents and voltages correspond to the measured values obtained in the experiment? Note any differences and note what the different resistances were on each side of the resistor  $R_{pot}$ , were the resistor values drastically different (more than  $100\Omega$  apart.)?

**Note:** When plotting the frequency response curves make sure the x and y axes are log (i.e., 1, 10, 100, 1000, etc.).