

Control Number: \_\_\_\_\_


Electrical and Computer Engineering  
**COMPREHENSIVE/BREADTH EXAM**

TTG Area: Comm., Ctrls., and Sig. Proc.

ECGR 4111: Control Systems

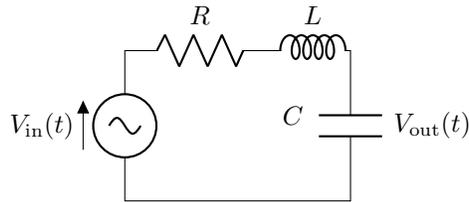**Solve either Problem 1 or Problem 2.**

Let  $I(t)$  denote the current in the following series RLC circuit:



The initial voltage across the capacitor and the initial current in the inductor are 0. The voltage equation for the circuit is

$$L \frac{dI(t)}{dt} + RI(t) + \frac{1}{C} \int_0^t I(\tau) d\tau = V_{in}(t), \quad (1)$$

where  $V_{in}(t)$  is the input to the circuit and  $V_{out}(t)$  (i.e., the voltage across the capacitor) is the output.

Some Useful Formulas

A linear system  $\dot{X} = AX + BU$ ,  $Y = CX + DU$  is *controllable* if

$$\text{rank}([B, AB, \dots, A^{n-1}B]) = n,$$

where  $n$  is the dimension of the state  $X$ .

The linear system is *observable* if

$$\text{rank} \left( \begin{bmatrix} C \\ CA \\ \vdots \\ CA^{n-1} \end{bmatrix} \right) = n.$$

For a second order transfer function of the form  $G(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$ , the bandwidth formula is

$$\text{BW} = \omega_n (1 - 2\zeta^2 + \sqrt{(1 - 2\zeta^2)^2 + 1})^{\frac{1}{2}}$$

The Resonant peak ( $M_r$ ) formula is

$$M_r = \begin{cases} \frac{1}{2\zeta\sqrt{1-\zeta^2}}, & \zeta < \frac{1}{\sqrt{2}} \\ 1, & \text{otherwise.} \end{cases}$$

1. (100 points) State-space analysis.

- (a) (30 points) For the given circuit, derive a state-space formulation of the following form:

$$\begin{aligned}\dot{X}(t) &= AX(t) + BV_{\text{in}}(t) \\ V_{\text{out}}(t) &= CX(t) + DV_{\text{in}}(t),\end{aligned}$$

where  $X(t) \in \mathbb{R}^2$ . Clearly define your choice of  $X(t)$ ,  $A$ ,  $B$ ,  $C$  and  $D$ .

- (b) (20 points) Check the stability of the system and determine whether the system is *marginally stable*/ *asymptotically stable*/ *unstable*.
- (c) (5 points) Is it possible to pick  $R, L, C$  to make the system unstable? If yes, provide an example. If no, prove your claim.
- (d) (5 points) Is it possible to pick  $R, L, C$  to make the system marginally stable? If yes, provide an example. If no, prove your claim.
- (e) (10 points) For your choice of  $A, B, C, D$ , determine whether the system is controllable?
- (f) (10 points) For your choice of  $A, B, C, D$ , determine whether the system is observable?
- (g) (20 points) Design a state feedback controller  $V_{\text{in}}(t) = -KX$  to place the eigenvalues of the closed-loop system at  $-1$  and  $-2$  respectively. Express  $K$  in terms of  $R, L$ , and  $C$ .

2. (100 points) Frequency Domain analysis.

- (a) (15 points) Compute the resonant peak  $M_r$  for the given RLC circuit.
- (b) (15 points) Keeping  $L$  and  $C$  fixed, if we vary  $R$ , how does  $M_r$  change with  $R$  (e.g., does  $M_r$  increase when  $R$  is increased etc.)?
- (c) (15 points) Find the Bandwidth (BW) of the RLC circuit.
- (d) (15 points) Suppose you cannot change  $R$ , but you may pick  $L$  and  $C$ . How would you choose  $L$  and  $C$  to maximize the bandwidth of the system?
- (e) (20 points) Let the input be  $V_{\text{in}}(t) = \sin(t) \cos^2(t)$ . What would be the steady-state output  $V_{\text{out}}(t)$  for this input?
- (f) (20 points) Design a Proportional-derivative (PD) feedback controller to place the poles of the closed-loop system at  $-1$  and  $-2$ . Express the gains  $K_p$  and  $K_d$  in terms of  $R, L$  and  $C$ .