

**Department of Electrical and Computer Engineering**  
**Breadth Exam / Comprehensive Exam**

Problems -----

Power Systems Area

ECGR 4141: Power System Analysis I

A 115 kV<sub>LL</sub>, 60-Hz 3-phase transmission line is 120 km long. It may be considered as a “*medium*” length line and represented as a nominal- $\pi$  model. The line has the following known parameters per phase:

$$z = (0.06 + j0.56) \Omega/\text{km}$$

$$y = (0 + j6.1 \times 10^{-6}) \text{ S/km to neutral.}$$

The line delivers 140 MVA at 120 kV (L-L) with a power factor of 0.8 lagging at the receiving end of the line.

- (a) (40 pts) Find the A, B, C, and D constants of the line. Mention units for all quantities as appropriate.
  
- (b) (35 pts) Find the sending end voltage magnitude  $V_S$  in kV<sub>LN</sub>.
  
- (c) (25 pts) Find per cent voltage regulation.